

## EE2026 (Part 1) Tutorial 3 - Questions

### Boolean Algebra Manipulation and Logic gates

- Boolean algebra is ultimately described by
  - a set of elements  $B=\{0,1\}$  (binary symbols) ← binary constants or variables (as in common algebra)
  - operator  $\neg$  (NOT) on single operand ← priority: NOT has highest precedence, followed by AND and OR  
→  $\neg(A \cdot B + C) = \neg((A \cdot B) + C)$
  - operators  $\cdot$  (AND),  $+$  (OR) on multiple operands ←  $\cdot$  has precedence over  $+$

- Closure
  - $\forall x, y \in B, x + y \in B$  (outcome of operation is still in B, obviously)
  - $\forall x, y \in B, x \cdot y \in B$  (outcome of operation is still in B, obviously)
- Neutral elements of  $+$  and  $\cdot$ 
  - There exists a 0 and 1 element in B, such that
    - $x + 0 = x$  ← 0 is neutral elements for  $+$
    - $x \cdot 1 = x$  ← 1 is neutral elements for  $\cdot$
- Commutative Law
  - $x + y = y + x$
  - $x \cdot y = y \cdot x$
- Distributive Law
  - $x \cdot (y + z) = x \cdot y + x \cdot z$  ( $\cdot$  over  $+$ , easy to remember)
  - $x + (y \cdot z) = (x + y) \cdot (x + z)$  ( $+$  over  $\cdot$  not intuitive, still true) } duality
- Complement
  - $\forall x \in B$ , there exists an element  $\bar{x} \in B$  (complement of  $x$ ) such that
    - $x + \bar{x} = 1$
    - $x \cdot \bar{x} = 0$
- There exist at least two distinct elements in the set  $B$  (obvious, it was introduced for more general algebras with more than two symbols)

#	Theorem		
1	$A + A = A$	$A \cdot A = A$	Tautology Law
2	$A + 1 = 1$	$A \cdot 0 = 0$	Union Law
3	$\overline{(\bar{A})} = A$		Involution Law
4	$A + (B + C) = (A + B) + C$	$A \cdot (B \cdot C) = (A \cdot B) \cdot C$	Associative Law
5	$\overline{A + B} = \bar{A} \cdot \bar{B}$	$\overline{A \cdot B} = \bar{A} + \bar{B}$	De Morgan's Law
6	$A + A \cdot B = A$	$A \cdot (A + B) = A$	Absorption Law
7	$A + \bar{A} \cdot B = A + B$	$A \cdot (\bar{A} + B) = A \cdot B$	
8	$AB + \bar{A}\bar{B} = A$	$(A + B)(\bar{A} + \bar{B}) = A$	Logical adjacency
9	$AB + \bar{A}C + BC = AB + \bar{A}C$	$(A + B)(\bar{A} + C)(B + C) = (A + B)(\bar{A} + C)$	Consensus Law

↔ duality (swap OR and AND, swap 0 and 1)

- A Boolean expression can be rewritten in many formally different (but equivalent) forms

- Sum of products (SOP)
  - Logic sum of product terms
  - Example:

$$F_1(A, B, C) = \overline{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}C$$

sum  
 ↕  
 products

- Product of sums (POS)
  - Logic product of sum terms
  - Example:

$$F_2(A, B, C) = (A + B + C) \cdot (A + \bar{B} + \bar{C}) \cdot (\bar{A} + B + C) \cdot (\bar{A} + \bar{B} + C) \cdot (\bar{A} + \bar{B} + \bar{C})$$

product  
 ↕  
 sums

## Boolean Algebra Manipulation and Logic gates

- Use algebraic manipulation to find the most simplified expression (MSOP, minimum SOP) for

$$F = x_1x_3 + x_1\bar{x}_2 + \bar{x}_1x_2x_3 + \bar{x}_1\bar{x}_2\bar{x}_3$$

Write the Verilog code that describes the above function as a module (use dataflow description style).

$F =$

$$\begin{aligned} & x_1x_3 + x_1\bar{x}_2 + \bar{x}_1x_2x_3 + \bar{x}_1\bar{x}_2\bar{x}_3 \\ &= x_3(x_1 + \bar{x}_1x_2) + \bar{x}_2(x_1 + \bar{x}_1\bar{x}_3) \quad \text{distributive law} \\ &= x_3(x_1 + x_2) + \bar{x}_2(x_1 + \bar{x}_3) \quad \left\{ \text{using } A + \bar{A}B = A + B \right\} \quad \bar{A} \text{ is redundant here (Theorem 7)} \\ &= \underbrace{x_1x_3}_{\text{consensus law}} + \underbrace{x_2x_3}_{\text{consensus law}} + \underbrace{x_1\bar{x}_2}_{\text{consensus law}} + \underbrace{\bar{x}_2\bar{x}_3}_{\text{consensus law}} \\ &= x_1x_3 + x_2x_3 + \bar{x}_2\bar{x}_3 \quad \left\{ \text{using } AB + \bar{A}C + BC = AB + \bar{A}C; A \rightarrow x_3, B \rightarrow x_1, C \rightarrow \bar{x}_2 \right\} \\ &\text{or } x_1\bar{x}_2 + x_2x_3 + \bar{x}_2\bar{x}_3 \quad \left\{ \text{using } AB + \bar{A}C + BC = AB + \bar{A}C; A \rightarrow \bar{x}_2, B \rightarrow x_1, C \rightarrow x_3 \right\} \\ & \quad \quad \quad \boxed{\cancel{x_1x_3}} + \boxed{x_2x_3} + \boxed{x_1\bar{x}_2} + \boxed{\bar{x}_2\bar{x}_3} \end{aligned}$$

**module** func(x1,x2,x3,F);  
     **input** x1,x2,x3;  
     **output** F;  
     **assign** F = x1 & x3 | x1 & ~x2 | ~x1 & x2 & x3 | ~x1 & ~x2 & ~x3;  
     // no parentheses are needed  
**endmodule**

continuous  
assignment

wire



↓  
automatically  
evaluate order  
precedence.

• > + .

① Standardize logic system.

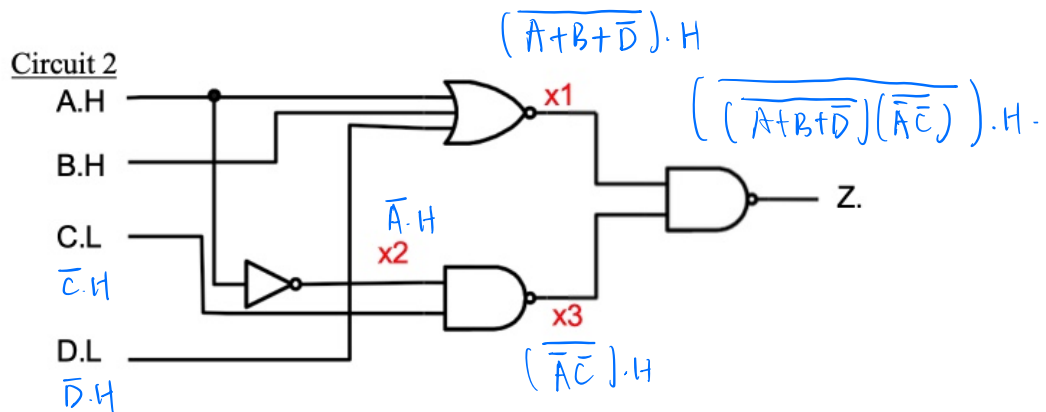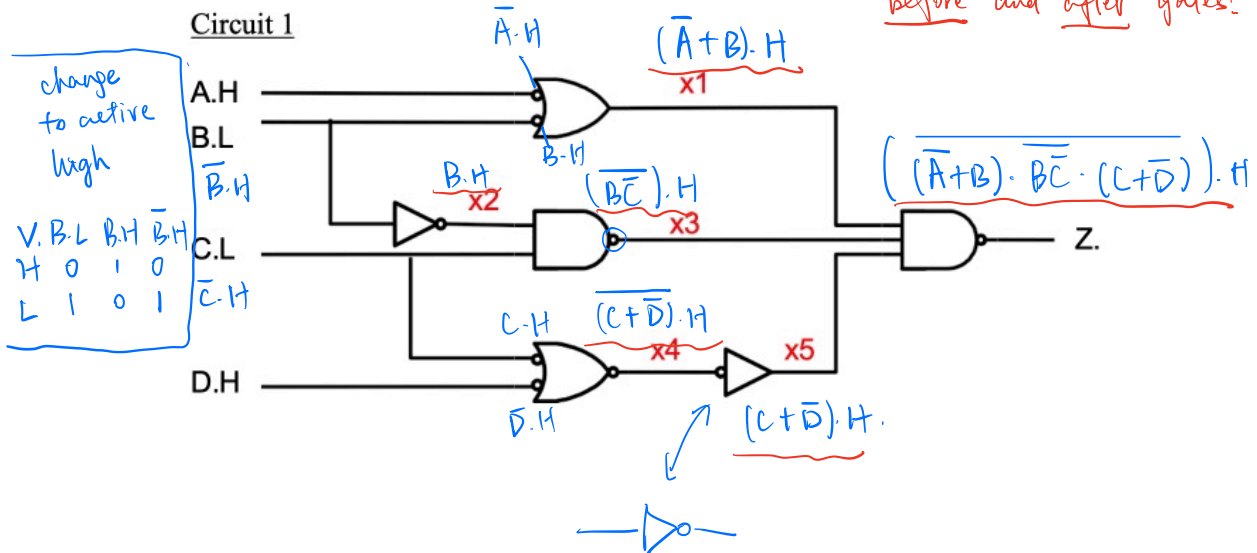2. Express all inputs and outputs as active high (i.e., complement active-low signals). The resulting circuit is in positive logic, and the expression of all intermediate nodes  $x1...x5$  is found immediately by proceeding from inputs to output: ② evaluate one by one

Evaluate each bubble  
before and after gates!



describe gates in Verilog

- (c) Using (structural modeling style) write the Verilog code that describes Circuit 2.  
2. Assume that Verilog primitives are available: not(out,in), nand(out,in1,in2,...), nor(out,in1,in2,...).

```


module func(Z,A,B,C,D); // Cb and Db are complemented (active-low)
    input A, B, C, D;
    output Z;
    wire x1, x2, x3, Cb, Db;
    not u1(Cb,C); // inverter gate to generate Cb=NOT(C) (see omitted inverter)
    not u2(Db,D); // inverter gate to generate Db=NOT(D) (see omitted inverter)
    nor u3(x1,A,B,Db); // NOR3 gate, instance u3
    not u4(x2,A); // inverter gate
    nand u5(x3,x2,Cb); // NAND2 gate
    nand u6(Z,x1,x3); // NAND2 gate
endmodule

```

gate type → voltage logic values.

	A	B	C	D	Cb	Db
X.H	L	L	L	L	0	0
X.L	L	L	L	L	0	0
	L	L	L	L	0	0
	L	L	L	L	0	0

 omitted inverter gates  
Cb:  $\bar{C}.H / C.L$   
Db:  $\bar{D}.H / D.L$



3. Design a logic circuit implementing the following Boolean function, using a minimum number of NOR gates. NOT gates can also be used if required.

$$X = A \oplus B \oplus C,$$


where  $\oplus$  represents the 2-operand XOR operation.

Use alternate gate representation if necessary for clear circuit diagrams.

$$(A\bar{B} + \bar{A}B) \oplus C \rightarrow D\bar{C} + \bar{D}C$$

$$X = A \oplus B \oplus C = (A\bar{B} + \bar{A}B) \cdot \bar{C} + (\bar{A}\bar{B} + A\bar{B}) \cdot C = A\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}\bar{B}C + ABC$$

$$A \oplus B = A\bar{B} + \bar{A}B$$

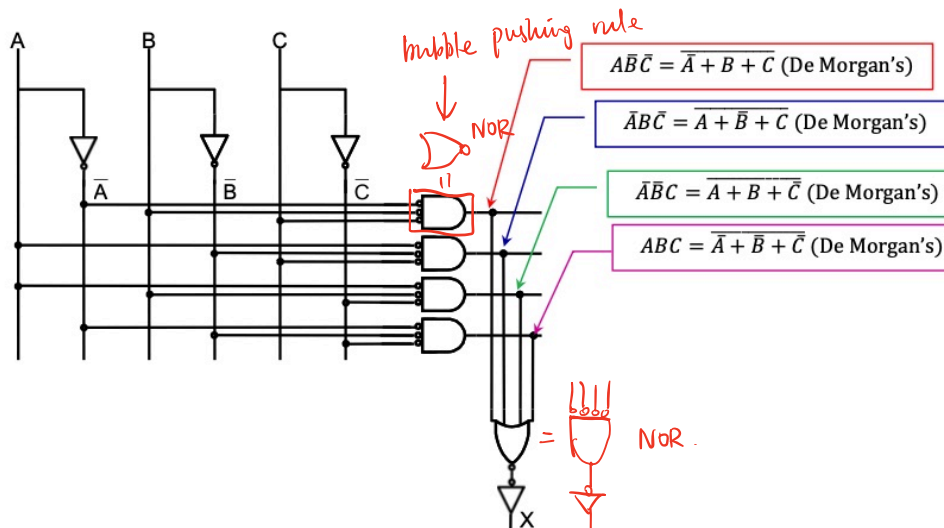

$$Z.H = (\bar{A}B + \bar{B}\bar{C}D + \bar{B}\bar{D}).H$$

4. Design a circuit to realize  $Z = \bar{A}B + \bar{B}\bar{C}D + \bar{B}\bar{D}$  in the positive logic convention.

A.L. B.L

C.H, D.H, Z.H

A and B are active low signals while C, D and Z are active high


Use a minimum of number of **only NAND** or **only NOR gates**. You may assume that the gates have no limits on the number of inputs. NOT gates can be used if required.

Draw clear circuit diagrams with alternate gate representations where necessary.


$$\star A.L = \bar{A}.H$$




Using NOR gates only:

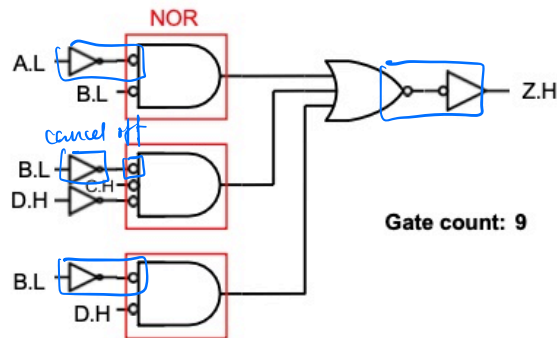

All NOR gates + Not gates (inverters)

 

Using NAND gates only:

 

All NAND gates + Not gates (inverters)

## 5. [Verilog Behavioural Style Modeling]

In the EE2026 design project, an OLED screen with 16-bit RGB colour resolution is used as a display device. The 16-bit signal colour resolution is represented through 5 bits for the red colour component, 6 bits for the green colour component, and 5 bits for the blue colour component. Write a Verilog program to switch between 4 display colours according to the table below.



The program receives a 2-bit input named SEL and produces a 16-bit output signal named PIXEL\_COLOUR.

SEL	Colour To Display	PIXEL_COLOUR
"00"	Red	"11111 000000 00000"
"01"	Blue	"00000 000000 11111"
"10"	Green	"00000 111111 00000"
"11"	Magenta	"11111 000000 11111"

high level  
behavioral  
data flow  
structural  
low level

### // Solution 1a - Behavioral Style of Modeling using if-else statements

```
module oled (input [1:0] SEL, output reg [15:0] PIXEL_COLOUR);
    always @ (SEL)
    begin
        if ( SEL[1] == 0 && SEL[0] == 0 )
            PIXEL_COLOUR = {5'b11111, 6'b000000, 5'b000000};
        else if ( SEL[1] == 0 && SEL[0] == 1 )
            PIXEL_COLOUR = {5'b00000, 6'b000000, 5'b11111};
        else if ( SEL[1] == 1 && SEL[0] == 0 )
            PIXEL_COLOUR = {5'b00000, 6'b111111, 5'b00000};
        else
            PIXEL_COLOUR = { 5'b11111, 6'b000000, 5'b11111};
    end
endmodule
```

procedural assignment

equivalence of  
procedural and  
continuous assign  
(L3. pg 17)

### // Solution 1b - Behavioral Style of Modeling using case statements

```
always @ (*)
begin
    case ({SEL[1],SEL[0]})
        2'b00 : PIXEL_COLOUR = 16'hF800;
        2'b01 : PIXEL_COLOUR = 16'h001F;
        2'b10 : PIXEL_COLOUR = 16'h07E0;
        2'b11 : PIXEL_COLOUR = 16'hF81F;
        default : PIXEL_COLOUR = 16'h0000;
        //the default statement is used to capture all other cases!
    endcase
end
```

continuous assignment

### // Solution 2 - Dataflow Style of Modeling using continuous assignments

```
assign PIXEL_COLOUR = (SEL[1]) ? ( (SEL[0] ? 16'hF81F : 16'h07E0) :
    (SEL[0] ? 16'h001F : 16'hF800);
```

wire  
check left bit

conditional operator  
(similar to C...)

check left bit {  
1: check right bit {  
0: check right bit {