

EE2026 (Part 1)
Tutorial 4 - Questions

Circuit Design

behaviour (truth table)



logic gates

Boolean expression.
(Minimization)

Boolean Algebra and Minimization

$A = 0 \Leftrightarrow \bar{A}$

$A = 1 \Leftrightarrow \bar{\bar{A}}$

A	B	C	minterm
0	0	0	$\bar{A} \cdot \bar{B} \cdot \bar{C}$
0	0	1	$\bar{A} \cdot \bar{B} \cdot C$
0	1	0	$\bar{A} \cdot B \cdot \bar{C}$
0	1	1	$\bar{A} \cdot B \cdot C$
1	0	0	$A \cdot \bar{B} \cdot \bar{C}$
1	0	1	$A \cdot \bar{B} \cdot C$
1	1	0	$A \cdot B \cdot \bar{C}$
1	1	1	$A \cdot B \cdot C$

input value making
minterm = 1

One-to-One
mapping

$|ABC| \Leftrightarrow \text{minterm} = 1$
 $|AB\bar{C}| \Leftrightarrow \text{maxterm} = 0$

A	B	C	maxterm
0	0	0	$A + B + C$
0	0	1	$A + B + \bar{C}$
0	1	0	$A + \bar{B} + C$
0	1	1	$A + \bar{B} + \bar{C}$
1	0	0	$\bar{A} + B + C$
1	0	1	$\bar{A} + B + \bar{C}$
1	1	0	$\bar{A} + \bar{B} + C$
1	1	1	$\bar{A} + \bar{B} + \bar{C}$

input value making
maxterm = 0

Convert Truth Table → Canonical Form: SOP (CSOP)

- In n-variable function, there are 2^n different minterms and maxterms
 - Example with n=3: sum of 4 products (CSOP)

A	B	C	F	minterm	maxterm
0	0	0	0	$\bar{A} \cdot \bar{B} \cdot \bar{C}$	$A + B + C$
0	0	1	0	$\bar{A} \cdot \bar{B} \cdot C$	$A + B + \bar{C}$
0	1	0	1	$\bar{A} \cdot B \cdot \bar{C}$	$A + \bar{B} + C$
0	1	1	0	$\bar{A} \cdot B \cdot C$	$A + \bar{B} + \bar{C}$
1	0	0	1	$A \cdot \bar{B} \cdot \bar{C}$	$\bar{A} + B + C$
1	0	1	1	$A \cdot \bar{B} \cdot C$	$\bar{A} + B + \bar{C}$
1	1	0	0	$A \cdot B \cdot \bar{C}$	$\bar{A} + \bar{B} + C$
1	1	1	1	$A \cdot B \cdot C$	$\bar{A} + \bar{B} + \bar{C}$

minterm: basic building block.
for $F=1$ in truth table

$$F = \bar{A} \cdot B \cdot \bar{C} + \bar{A} \cdot B \cdot C + A \cdot \bar{B} \cdot \bar{C} + A \cdot \bar{B} \cdot C$$

any minterm = 1, $F=1$.
if no minterm = 1, $F=0$

- Truth table is expressed directly with canonical form by
 - Identifying minterms = 1 for the input values making $F=1$
 - (Logically) add them up

Convert Truth Table → Canonical Form: POS (CPOS)

- Example with n=3: product of 3 sums (CPOS)

A	B	C	F	minterm	maxterm
0	0	0	0	$\bar{A} \cdot \bar{B} \cdot \bar{C}$	$A + B + C$
0	0	1	0	$\bar{A} \cdot \bar{B} \cdot C$	$A + B + \bar{C}$
0	1	0	1	$\bar{A} \cdot B \cdot \bar{C}$	$A + \bar{B} + C$
0	1	1	0	$\bar{A} \cdot B \cdot C$	$A + \bar{B} + \bar{C}$
1	0	0	1	$A \cdot \bar{B} \cdot \bar{C}$	$\bar{A} + B + C$
1	0	1	0	$A \cdot \bar{B} \cdot C$	$\bar{A} + B + \bar{C}$
1	1	0	0	$A \cdot B \cdot \bar{C}$	$\bar{A} + \bar{B} + C$
1	1	1	1	$A \cdot B \cdot C$	$\bar{A} + \bar{B} + \bar{C}$

maxterm: basic building block for $F=0$.

any maxterm = 0, $F=0$


no maxterm = 0, $F=1$

$$F = (A + B + C) \cdot (A + B + \bar{C}) \cdot (A + \bar{B} + C) \cdot (A + \bar{B} + \bar{C})$$

each maxterm is 0 only for a specific input
(no "interference" with other inputs)
→ just multiply maxterms independently

- Truth table is expressed directly with canonical form by
 - Identifying maxterms = 0 for the input values making $F=0$
 - (Logically) multiply them

Two-variable K-map:
(maximum 4 minterms)

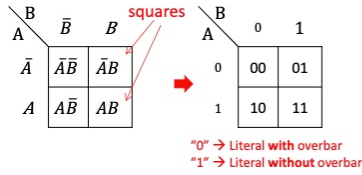

$m_0 \rightarrow 00 \rightarrow \bar{A}\bar{B}$
 $m_1 \rightarrow 01 \rightarrow \bar{A}B$
 $m_2 \rightarrow 10 \rightarrow A\bar{B}$
 $m_3 \rightarrow 11 \rightarrow AB$

Compress
Truth Table → K-map.

A, B. Cols → A row
B col.

Three-variable K-map

BC	$\bar{B}\bar{C}$	$\bar{B}C$	$B\bar{C}$	BC
\bar{A}	$\bar{A}\bar{B}\bar{C}$	$\bar{A}\bar{B}C$	$\bar{A}B\bar{C}$	$\bar{A}BC$
A	$A\bar{B}\bar{C}$	$A\bar{B}C$	$AB\bar{C}$	ABC

BC	00	01	11	10
0	000	001	011	010
1	100	101	111	110

BC	00	01	11	10
0	m_0	m_1	m_3	m_2
1	m_4	m_5	m_7	m_6

Four-variable K-map

CD	00	01	11	10
00	0000	0001	0011	0010
01	0100	0101	0111	0110
11	1100	1101	1111	1110
10	1000	1001	1011	1010

CD	00	01	11	10
00	m_0	m_1	m_3	m_2
01	m_4	m_5	m_7	m_6
11	m_{12}	m_{13}	m_{15}	m_{14}
10	m_8	m_9	m_{11}	m_{10}

A	B	F
0	0	0
0	1	0
1	0	1
1	1	1

$F = \bar{A}B + AB\bar{C} + \bar{A}\bar{B}C$

$\bar{A}B = \bar{A}B(C + \bar{C}) = \bar{A}BC + \bar{A}B\bar{C}$

BC	00	01	11	10
0	0	1	1	1
1	0	0	0	1


$F = A + \bar{A}\bar{B}CD + B\bar{C}\bar{D}$

CD	00	01	11	10
00	0	0	1	0
01	1	0	0	0
11	1	1	1	1
10	1	1	1	1

Or $\bar{A}B \rightarrow 01, C = 0 \text{ or } 1$

SOP → MSOP : group "1"s

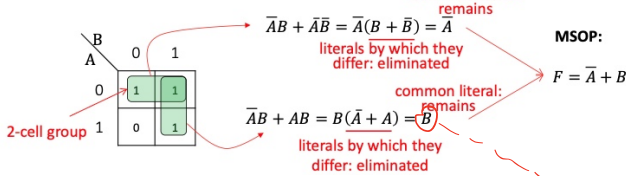Simplify: $F = \bar{A}B + AB + \bar{A}\bar{B}$



CD	00	01	11	10
00	1	0	0	1
01	X	1	X	1
11	X	1	X	1
10	1	0	0	1

Assume $X = 1$

group as big as possible.
can overlap.

Grouping: looking for the unchanged Boolean expression

Don't care X.
place holder.
can be 1.

two variable change value

CD	00	01	11	10
00	1	0	1	0
01	0	1	1	0
11	0	1	1	0
10	1	0	1	0

CD	00	01	11	10
00	1	0	0	1
01	0	1	1	0
11	0	1	1	0
10	1	0	0	1

CD	00	01	11	10
00	1	0	1	0
01	0	1	1	0
11	0	1	1	0
10	1	0	1	0

Squares in the group are not in power of two

CD	00	01	11	10
00	0	1	0	1
01	1	0	0	1
11	0	1	1	1
10	0	1	1	1

not horizontal or vertical

no boundary.
all connected. (POS → MPOS: group "0"s, X can be 0.)


1. A switching circuit has four inputs as shown. A and B represent the MSB and LSB bits of a binary number N_1 . C and D represent the MSB and LSB bits of a binary number N_2 . The output is to be 1 only if the product $N_1 \times N_2$ is less than or equal to 2. *decimal*.

(a) Write the truth table for the system.

(b) Write the canonical SOP and POS expressions for F .

(c) Draw a Karnaugh-map (K-map) for the function F .

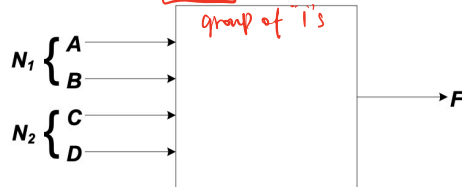(d) From the K-map, derive the MSOP expression for F .



$$N_1 = (AB)_2$$

$$N_2 = (CD)_2$$

$$\text{if } N_1 \times N_2 \leq 2 : F = 1$$

$$\text{else: } F = 0.$$

Truth Table

A	B	C	D	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

$$1 \times 3 > 2.$$

$$2 \times 2 > 2$$

$$2 \times 3 > 2$$

$$3 \times 1 > 2$$

$$3 \times 2 > 2$$

$$3 \times 3 > 2$$

(F=1)

$$Z_{SOP} = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}CD + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + \bar{A}BC\bar{D} + \bar{A}BCD + A\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}D + AB\bar{C}\bar{D} + ABC\bar{D}$$

(F=0)

$$Z_{POS} = (A + \bar{B} + \bar{C} + \bar{D}).(\bar{A} + B + \bar{C} + D).(\bar{A} + B + \bar{C} + \bar{D}).(\bar{A} + \bar{B} + C + \bar{D}).(\bar{A} + \bar{B} + C + D).(\bar{A} + \bar{B} + \bar{C} + D).$$

$X=0 \leftrightarrow \bar{X}$
verify minterm

$X=0 \leftrightarrow X.$
verify maxterm

AB \ CD	00	01	11	10
00	1	1	1	1
01	1	1	0	1
11	1	0	0	0
10	1	1	0	0

simplify (save logic gates)

$$Z_{MSOP} = \bar{A}\bar{B} + \bar{C}\bar{D} + \bar{A}\bar{C} + \bar{A}\bar{D} + \bar{B}\bar{C}$$

groups with 2 "1"s.

2. A bank vault has three locks with a different key for each lock. Each key is owned by a different person. To open the door, at least two people must insert their keys into the assigned locks. The signal lines A , B and C are 1 if there is a key inserted into lock 1, 2 or 3, respectively. Write an equation for the variable Z which is 1 if and only if the door should open.
- Write the truth table for the system.
 - Write the canonical SOP and POS expressions for Z .
 - Draw a Karnaugh-map (K-map) for the function Z .
 - From the K-map, derive the MSOP expression for Z .

Truth Table

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$F=1$

$F=0$

$$Z_{SOP} = \bar{A}BC + A\bar{B}C + ABC\bar{C} + ABC$$

$$Z_{POS} = (A + B + C) \cdot (A + B + \bar{C}) \cdot (A + \bar{B} + C) \cdot (\bar{A} + B + C)$$

		A	
BC		0	1
00		0	0
01		0	1
11		1	1
10		0	1

$$Z_{MSOP} = AC + BC + AB$$

SOP: $X=1 \leftrightarrow X$
 $X=0 \leftrightarrow \bar{X}$

3. Use K-maps to obtain an MSOP and an MPOS for each of the following functions:

(a) $Z = \overline{A}\overline{B}\overline{C}D + \overline{A}B\overline{C}D + A\overline{B}\overline{C}D + A\overline{B}CD + \overline{A}B\overline{C}\overline{D}$ with don't care for $ABCD = 1010$

(b) $Z = (\overline{A} + B + \overline{C})(A + B + \overline{C})$ with don't cares for $ABC = 111$ and 110

(c) $f(x_1, \dots, x_4) = \sum m(0, 4, 5, 6, 7) + D(1, 12, 13, 14, 15)$, where $m()$ is the set of minterms for which $f=1$ and $D()$ is the set of don't cares. For example, $m(2)$ is the minterm corresponding to $x_1x_2x_3x_4 = 0010$ (this alternate shorthand notation is often used to express SOPs).

(a) $Z = \overline{A}\overline{B}\overline{C}D + \overline{A}B\overline{C}D + A\overline{B}\overline{C}D + A\overline{B}CD + \overline{A}B\overline{C}\overline{D}$ with 'X' for $ABCD = 1010$

		AB			
		00	01	11	10
CD	00	0	0	0	1
	01	1	1	1	1
	11	0	0	0	0
	10	0	0	0	X

MSOP

$$Z = \overline{C}D + A\overline{B}\overline{C}$$

group of 4
group of 2

MPOS

$$Z = \overline{C}(A+D) \cdot (\overline{B}+D)$$

group of 8
group of 4
group of 4

$X=1 \leftrightarrow \overline{X}$
 $X=0 \leftrightarrow X$
Verify using $C=1$.

		AB			
		00	01	11	10
CD	00	0	0	0	1
	01	1	1	1	1
	11	0	0	0	0
	10	0	0	0	X

(b) $Z = (\overline{A} + B + \overline{C})(A + B + \overline{C})$ with don't cares for $ABC = 111$ and 110

		A	
		0	1
BC	00	1	1
	01	0	0
	11	1	X
	10	1	X

MSOP

$$Z = B + \overline{C}$$

		A	
		0	1
BC	00	1	1
	01	0	0
	11	1	X
	10	1	X

MPOS

$$Z = (B + \overline{C})$$

all the rest are 1.

to binary!
0000 0100 0101 0110 0111

(c) $f(x_1, \dots, x_4) = \sum m(0, 4, 5, 6, 7) + D(1, 12, 13, 14, 15)$, where D is the set of don't cares and m is the set for which $f=1$ (this alternate shorthand notation is also used to express min terms).

		X_1X_2			
		00	01	11	10
X_3X_4	00	1	1	X	0
	01	X	1	X	0
	11	0	1	X	0
	10	0	1	X	0

MSOP

$$Z = (x_2 + \overline{x}_1\overline{x}_3)$$

		X_1X_2			
		00	01	11	10
X_3X_4	00	1	1	X	0
	01	X	1	X	0
	11	0	1	X	0
	10	0	1	X	0

MPOS

$$Z = (x_2 + \overline{x}_3) \cdot (\overline{x}_1)$$

4. A combinational circuit has four inputs A, B, C and D and one output Z. The output is asserted whenever three or more of the inputs are asserted, otherwise the output is de-asserted. Find an MSOP expression for Z. Design the combinational circuit using only inverters, 2-input NAND gates and 3-input NAND gates. Assume that A, B and Z are active high signals, while C and D are active low signals. Use alternate gate representations for clarity of circuit diagrams. Calculate the critical path delay.


Gate	t_{pd}
NOT	0.3ns
2-input NAND	0.5ns
3-input NAND	0.8ns

Handwritten: $ABCD$
 1110
 1101
 1011
 0111
 1111 } $Z=1$

AB \ CD	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	0	1	1	1
10	0	0	1	0

MSOP

$$Z = ACD + BCD + ABC + ABD$$

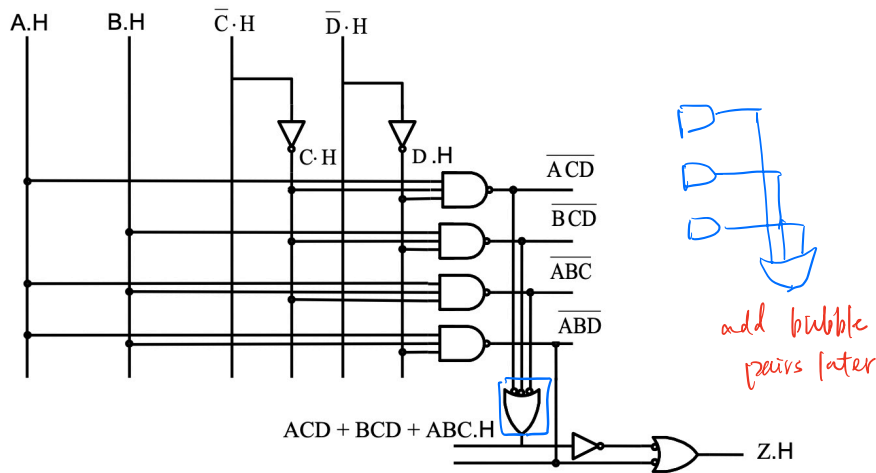

$$Z.H = (ACD + BCD + ABC + ABD).H$$

Critical Path Delay
 $= 0.3 \text{ (NOT)} + 0.8 \text{ (NAND3)} + 0.3 \text{ (NOT)} + 0.5 \text{ (NAND2)}$
 $= 2.7\text{ns}$

longest path (pass through the most gates)

$$\bar{C}.H \rightarrow Z.H$$