

EE2026

Digital Design

COMBINATIONAL LOGIC IN VERILOG

Massimo ALIOTO

Dept of Electrical and Computer Engineering

Email: massimo.alioto@nus.edu.sg

Get to know the latest silicon system breakthroughs from our labs in 1-minute video demos





Outline


- Combinational vs. sequential logic circuits
- Review of code snippets and common errors
- Continuous assignment
- Procedural assignment
- Equivalence of continuous and procedural assignment
- Structural design
- Testbenches

Combinational vs. Sequential Logic

  - Any digital system partitioned into combinational and sequential logic
- Combinational logic
 - Output at given time depends only on inputs at same time (apart from gate delays)
 - No memory



 - Sequential logic
 - Output at given time depends on inputs at same time and past inputs
 - Includes some form of memory elements (e.g., flip-flops, registers, memory)



Review of Code Snippets and Common Errors

Verilog level of abstraction

```
module box(input  a, b,
           input  [1:0] c,
           output [3:0] y );





  wire tmp;
  reg [1:0] one = 3;
  reg two;
  integer three = 1;

  assign y[3] = one[0];
  assign y[2:1] = a + c;
  assign y[0] = ( a > b );

endmodule
```

Net / Variable Name	Number of bits?	Value in dec / bin
a	1	1 / 1'b1
b	1	0 / 1'b0
c	2	2 / 2'b10
tmp	1	Z / 1'bZ
one	2	3 / 2'b11
two	1	X / 1'bX
three	32	1 / 32'h00000001
y	4	15 / 4'b1111

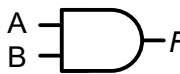gate level of abstraction

Gate	Symbol	Function (F)	Verilog Operator	Gate	Symbol	Function (F)	Verilog Operator
AND		$A \cdot B$	$F = A \& B$	NOT		\bar{A}	$F = \sim A$
OR		$A + B$	$F = A \mid B$	XOR		$A \oplus B$	$F = A \wedge B$

Boolean level of abstraction

```
assign F = ~w & ~x & z | ~w & x & z | w & y & z | x & y & z;
```

Review of Code Snippets and Common Errors


```
module notgood  
(...)
```

```
    reg z; ←  
    assign z = a | b;
```

```
endmodule
```

Assign statements are used only for wire or net types

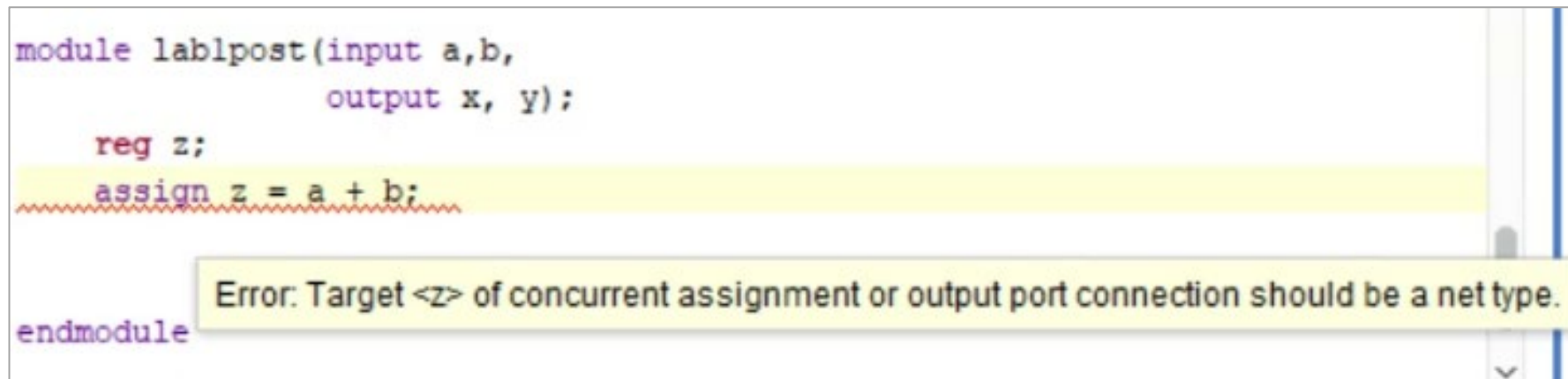→ error states that <z> signal should be a net type



Review of Code Snippets and Common Errors

```
module notgood(...);  
  
(...)
```

```
    assign x = a | b;  
    assign x = a + b;
```

There are two conflicting instructions (multi-driven net)


Signal x is connected to TWO “drivers”
→ Multiple Driver Nets error will occur

```
endmodule
```



Continuous Assignment

 - **assign** statements are used to model combinational logic



```
module bigbox (input a, b, c, d,
               output z);
```


```
  wire p, q, r;  internal connections
```

order?

irrelevant

```
  assign z = p ^ q ^ r; 1
  assign q = ~c;         2
  assign p = a & b;       3
  assign r = ~(c | d);   4
```


```
endmodule
```

 

- Whenever there is an event on the RHS signal, expression is evaluated and assigned (after Δ delay) → continuously updated (assigned)
- Multiple statements executed concurrently (in parallel)
- **wire** used to represent an internal (physical) connection

Continuous Assignment

 - **assign** statements can also be merged arbitrarily



```
module bigbox (input a, b, c, d,  
              output z);  
  
  assign Z = (a & b) ^ ~c ^ ~(c | d);  
  
endmodule
```

- Concurrently anyway, no sequence whatsoever

Useful Operators

- Boolean (bit-wise), logical, arithmetic, concatenation
 - Use brackets for readability, use only synthesizable statements (apart from testbenches)

<div style="display: flex; align-items: center;"> <div style="writing-mode: vertical-rl; transform: rotate(180deg);">precedence</div> <div style="margin-left: 10px;"> <div style="text-align: center;">↑</div> <div style="text-align: center;">high</div> <div style="text-align: center;">↓</div> <div style="text-align: center;">low</div> </div> </div>	Operator	Description	Examples: $a = 4'b1010$, $b = 4'b0000$	
	!, ~	Logical negation, Bit-wise NOT	!a = , !b = , ~a=4'b , ~b=4'b	if all bits=0 ("false vector") → 1 0 otherwise
	&, , ^	Reduction (merges all bits)	&a = , a = , ^a =	
	{ __, __ }	Concatenation	{b, a} = 8'b	
	{ n{ __ } }	Replication	{ 2 {a} } = 8'b	
	*, /, %	Multiply, *Divide, *Modulus	3 % 2 = 1, 16 % 4 = 0	
	+, -	Binary addition, subtraction	a + b = 4'b1010	
	<<, >>	Shift Zeros in Left / Right	a << 1 = 4b' , a >> 2 = 4'b	<< towards MSB (0s inserted) >> towards LSB (0s inserted)
	<, <=, >, >=	Logical Relative (1-bit output)	(a > b) =	(independent of index order)
	==, !=	Logical Equality (1-bit output)	(a == b) = (a != b) =	
	&, ^,	Bit-wise AND, XOR, OR	a&b = a b =	
	&&,	Logical AND, OR (1-bit output)	a&&b = a b =	vector 00...0 equivalent to 0 (1 otherwise)
	?:	Conditional Operator	<out> = <condition> ? If_ONE : if_ZERO	


Useful Operators

- Boolean (bit-wise), logical, arithmetic, concatenation
 - Use brackets for readability, use only synthesizable statements (apart from testbenches)


	Operator	Description	Examples: a = 4'b1010, b=4'b0000
<div>high</div> <div>↑</div> <div>precedence</div> <div>↓</div> <div>low</div>	!, ~	Logical negation, Bit-wise NOT	!a = 0, !b = 1, ~a = 4'b0101, ~b = 4'b1111
	&, , ^	Reduction (merges all bits)	&a = 0, a = 1, ^a = 0
	{ __, __ }	Concatenation	{b, a} = 8'b00001010
	{ n{ __ } }	Replication	{ 2 {a} } = 8'b10101010
	*, /, %,	Multiply, *Divide, *Modulus	3 % 2 = 1, 16 % 4 = 0
	+, -	Binary addition, subtraction	a + b = 4'b1010
	<<, >>	Shift Zeros in Left / Right	a << 1 = 4'b0100, a >> 2 = 4'b0010
	<, <=, >, >=	Logical Relative (1-bit output)	(a > b) = 1
	==, !=	Logical Equality (1-bit output)	(a == b) = 0 (a != b) = 1
	&, ^,	Bit-wise AND, XOR, OR	a & b = 4'b0000 a b = 4'b1010
	&&,	Logical AND, OR (1-bit output)	a && b = 0 a b = 1
	?:	Conditional Operator	<out> = <condition> ? If_ONE : if_ZERO

Conditional Operator

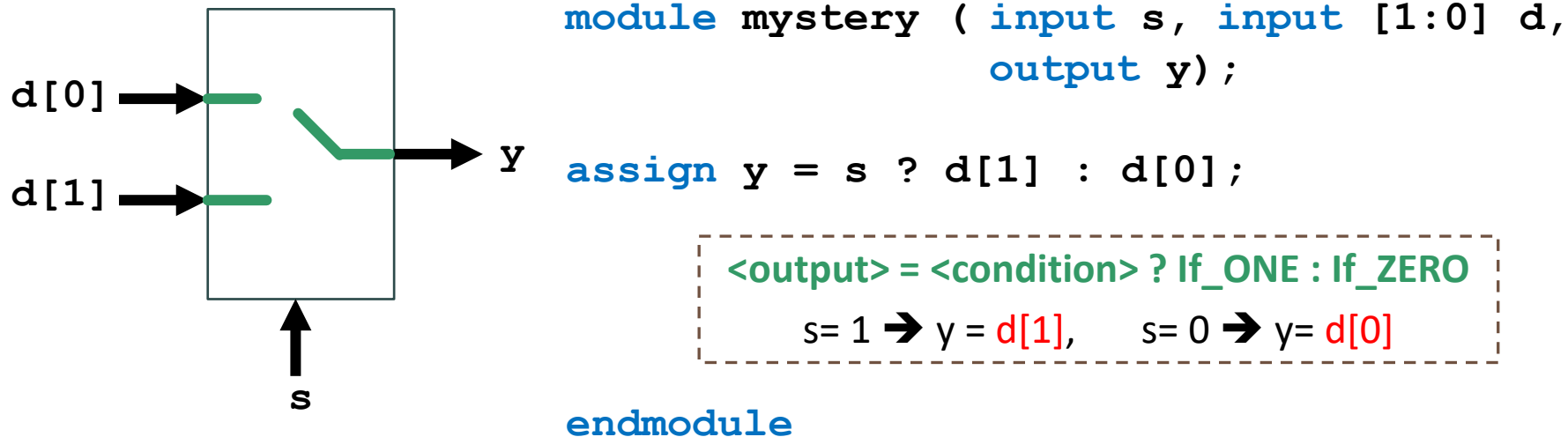- The `?:` conditional operator allows to select the output from a set of inputs based on a condition



 - This expression is evaluated whenever there is an event on any input
 - Continuous assignment
- What is this block? ← 2:1 multiplexer (MUX, see next week)



Procedural Assignment: always @


- Behavioral (higher-level description of logic)
 - Two assignment types: blocking vs. non-blocking

`y = d;`

expresses combinational logic

`y <= d;`

expresses sequential logic (see later)

 

```
module mux21 ( input s, input [1:0] d,
               output reg y );
```

anything assigned in an **always** block must be declared as type **reg**

```
always @ (s, d)
```

```
begin
```

```
  if (s == 1'b0)
    y = d[0];
  else
    y = d[1];
```

```
end
```

```
endmodule
```

conceptually, the **always** block runs *once* when any signal in *sensitivity list* (s,d) changes value

statements executed sequentially & evaluated instantaneously → order matters!

begin and **end** behave like parentheses/brackets for conditional statements.

Procedural Assignment: always @

- **always@(*)** for combinational logic
 - Sensitivity list must include **all input signals** that are read in current block
 - otherwise, no longer combinational: memory is inferred (see part II)
 - All outputs always explicitly assigned for any input value (including z, x...)
 - otherwise, no longer combinational: latch is inferred (see part II)
- Statements within always block are executed sequentially
 - But irrelevant with blocking assignments/combinational logic (see later for non-blocking)
- Multiple always blocks run concurrently (like continuous assignment)

```
always @ (...)    always @ (...)
begin              begin
...                ...
end                end
```

- No ~~assign~~ in always blocks

Review of Code Snippets and Common Errors

```
module notgood(...);  
    always @ (*)  
        y = y + 1;
```

```
    always @ (*)  
        y = y + 3;
```

```
endmodule
```



There are two conflicting instructions:

- first instruction would be to increment y by 1
- second would be to increment y by 3

Another case of multi-driven net (here with multiple procedural blocks)

 **Implementation** (5 errors)

 **Opt Design** (5 errors)

 [DRC 23-20] Rule violation (MDRV-1) Multiple Driver Nets - Net y_OBUF[0] has multiple drivers: y_reg[0],
 [Vivado_Tcl 4-78] Error(s) found during DRC. Opt_design not run.

Control-Flow Statements: Conditional

- Conditional statements: computations executed depending on conditions/value of variables

- Always within procedural block (**always @**)

- **if, if-else** and **else-if** 

- If expression evaluates to true → execute statement(s)
- Otherwise, do not (or else...)

If - else if - else

```
if ( expr )  
    statement;
```

```
if ( expr )  
    statement;  
else  
    statement;
```

- Nested **if-else** 

Nested if-else

```
if (cond1)        signal_name<=value1;  
else if (cond2)   signal_name<=value2;  
else if (cond3)   signal_name<=value3;  
...  
else              signal_name<=defaultvalue;
```

```
if ( expr )  
    statement;  
else if ( expr )  
    statement;  
else if ( expr )  
    statement;  
else  
    statement;
```

- Entails sense of priority
- Use it if intended
- If not, redundant logic is generated
 - unless conditions are mathematically guaranteed to be mutually exclusive

 **synthesis**

```
signal_name <= cond1*value1+not(cond1)*cond2*value2+...  
not(cond1)*not(cond2)*...*defaultvalue
```

Control-Flow Statements: Conditional

- Conditional statements: computations executed depending on conditions/value of variables

- Always within procedural block (**always @**)

- **case** compares expression with each case item

- If none match, the default statement is executed
- Default clause: unknown/unspecified values, shortens notation

case

case (expr)

value1 : statement;
value2 : statement;
value3 : statement;
...
default : statement;

endcase

- No priority implied (mutually exclusive values)

- logic checks only if expression matches one case item

case (an-1...a0)
item1: value1;
item2: value2;
...
itemn: valuen;

endcase

synthesis


- No redundant logic is generated

signal_name <= cond1*value1+cond2*value2+ ... condn*valuen

Equivalence of Procedural and Continuous Assign.

```
module mux21 ( input s, input [1:0] d, output reg y );

 always @ (s, d)
begin
    if (s == 1'b0)
        y = d[0];
    else
        y = d[1];
end
endmodule
```




```
module mux ( input s, input [1:0] d, output y );

assign y = s ? d[1] : d[0];

endmodule
```

 Equivalence of Procedural and Continuous Assign.



```
module bigbox
(input a,b,c,d, output z);

wire p, q, r;


assign q = ~c;
assign z = p ^ q ^ r;
assign p = a & b;
assign r = ~(c | d);

endmodule
```

```
module bigbox
(input a,b,c,d, output reg z);
reg p,q,r;
always @ ( a, b, c, d )
begin
    q = ~c;
    p = a & b;
    r = ~(c | d);
    z = p ^ q ^ r;
end
endmodule
```

Structural Modeling

 - Structural modeling connects modules and gates
 - Practice with equivalent dataflow and structural description styles



Dataflow

```
module bigbox (input a,b,c,d, output z);  
  
    assign z = (a & b) ^ ~c ^ ~(c | d) ;  
  
endmodule
```


Structural (using primitives)

```
module bigbox (input a,b,c,d, output z);  
    wire p, q, r;  
  
    and u1 (p, a, b); //output, then inputs  
    not u2 (q, c);  
    nor u3 (r, c, d);  
    xor u4 (z, p, q, r);  
  
endmodule
```


Structural Modeling

 - Examples: 2:1 MUX and 4:1 MUX

```
module mux21( input s,  
              input [1:0] d,  
              output y);  
  
    assign y = s ? d[1] : d[0];  
  
endmodule
```



 
```
module mux41( input [1:0] s,  
              input [3:0] d,  
              output y);  
  
    ... .. ?  
  
endmodule
```




Structural Modeling

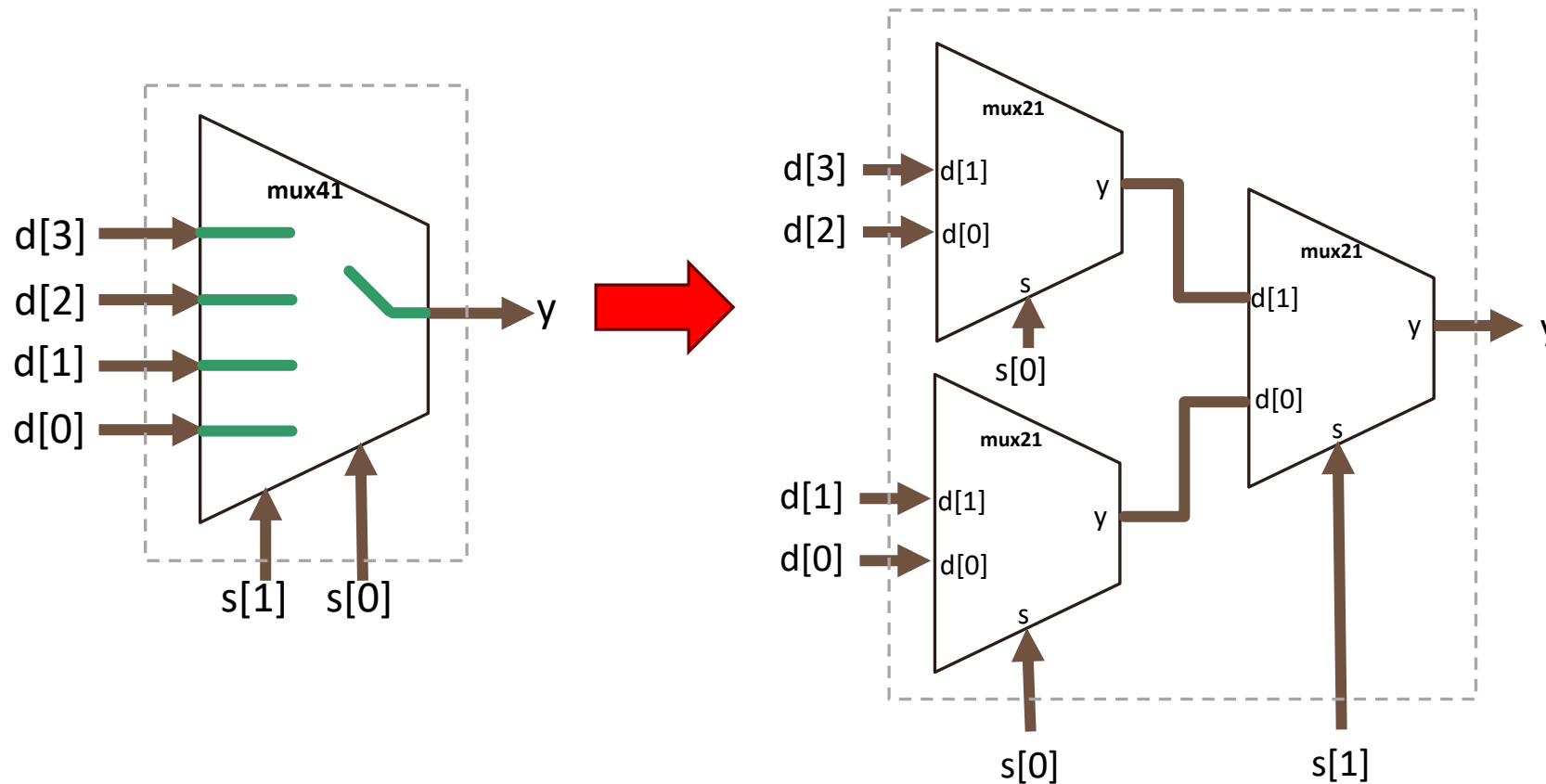- 4:1 multiplexer can also be implemented by combining several 2-to-1 multiplexers



Structural Modeling

 - 4:1 multiplexer can also be implemented by combining several 2-to-1 multiplexers




```
module mux21( input s, input [1:0] d,  
              output y);  
    assign y = s ? d[1] : d[0];  
endmodule
```

Port Connection by Position

```
module mux41( input [1:0] s,  
              input [3:0] d,  
              output y);  
  
    wire out1, out2;  
  
    //check for port order!  
    mux21 u1 (s[0], d[3:2], out1);  
  
    mux21 u2 (                );  
  
    mux21 u3 (                );  
  
endmodule
```

Structural Modeling

 - 4:1 multiplexer can also be implemented by combining several 2-to-1 multiplexers



```
module mux21( input s, input [1:0] d,
              output y);
    assign y = s ? d[1] : d[0];
endmodule
```

Port Connection by Position

```
module mux41( input [1:0] s,
              input [3:0] d,
              output y);

    wire out1, out2;

    //check for port order!
    mux21 u1 (s[0], d[3:2], out1);


    mux21 u2 ( s[0], d[1:0], out2 );

    mux21 u3 ( s[1], {out1, out2}, y );

endmodule
```

Structural Modeling

 - 4:1 multiplexer can also be implemented by combining several 2-to-1 multiplexers




Port Connection by Name


```
module mux41( input [1:0] s,  
              input [3:0] d,  
              output y);  
  
  wire out1, out2;  
  
  mux21 u1 (.s ( s[0]),  
            .d ( d[3:2] ),  
            .y ( out1 ) );  
  
  mux21 u2 (.s ( s[0]),  
            .d ( d[1:0] ),  
            .y ( out2 ) );  
  
  mux21 u3 (.s ( s[1]),  
            .d ( {out1, out2} ),  
            .y ( y ) );  
  
endmodule
```


Structural Modeling

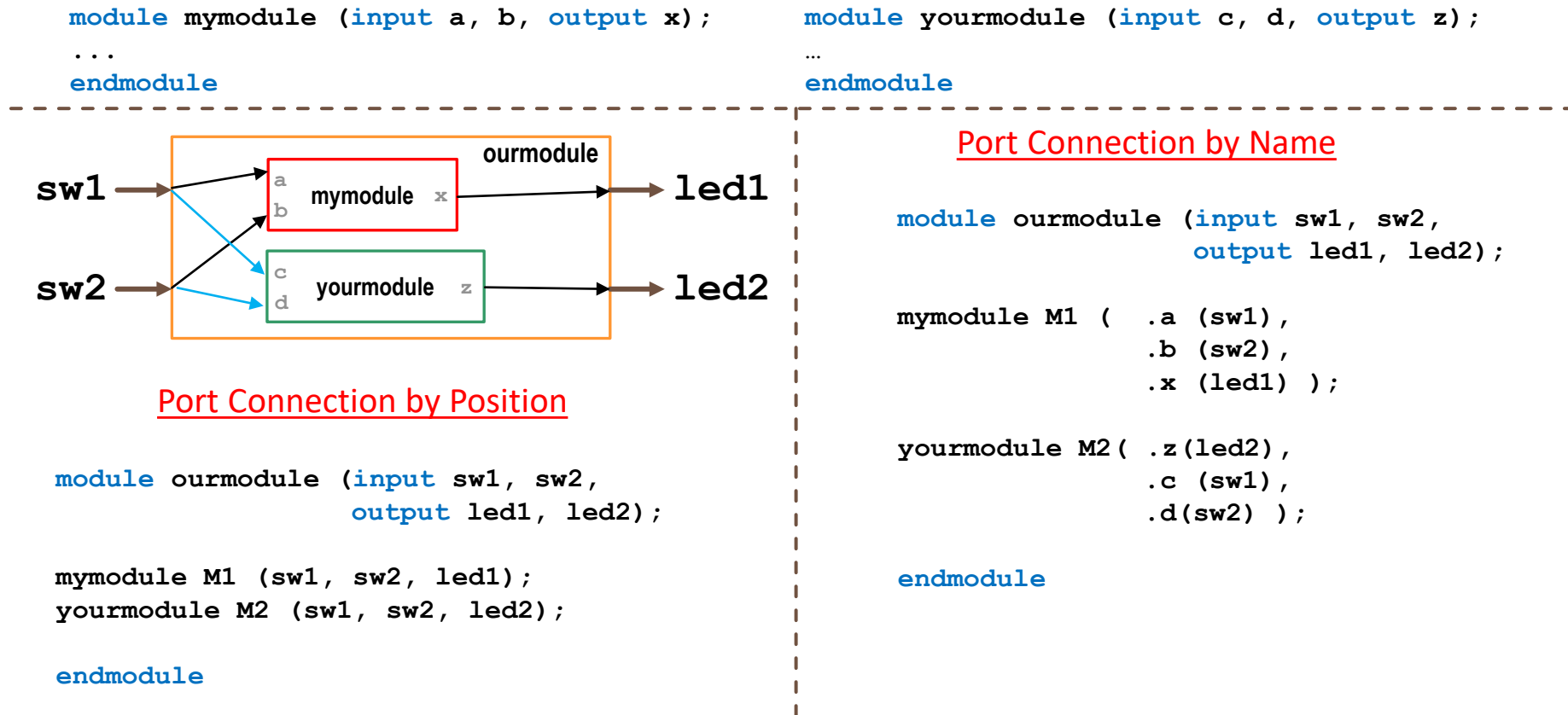- For modular designs, the top view is specified as interconnected blocks
 - these examples demonstrate port connection by position / name.



Logic Simulations

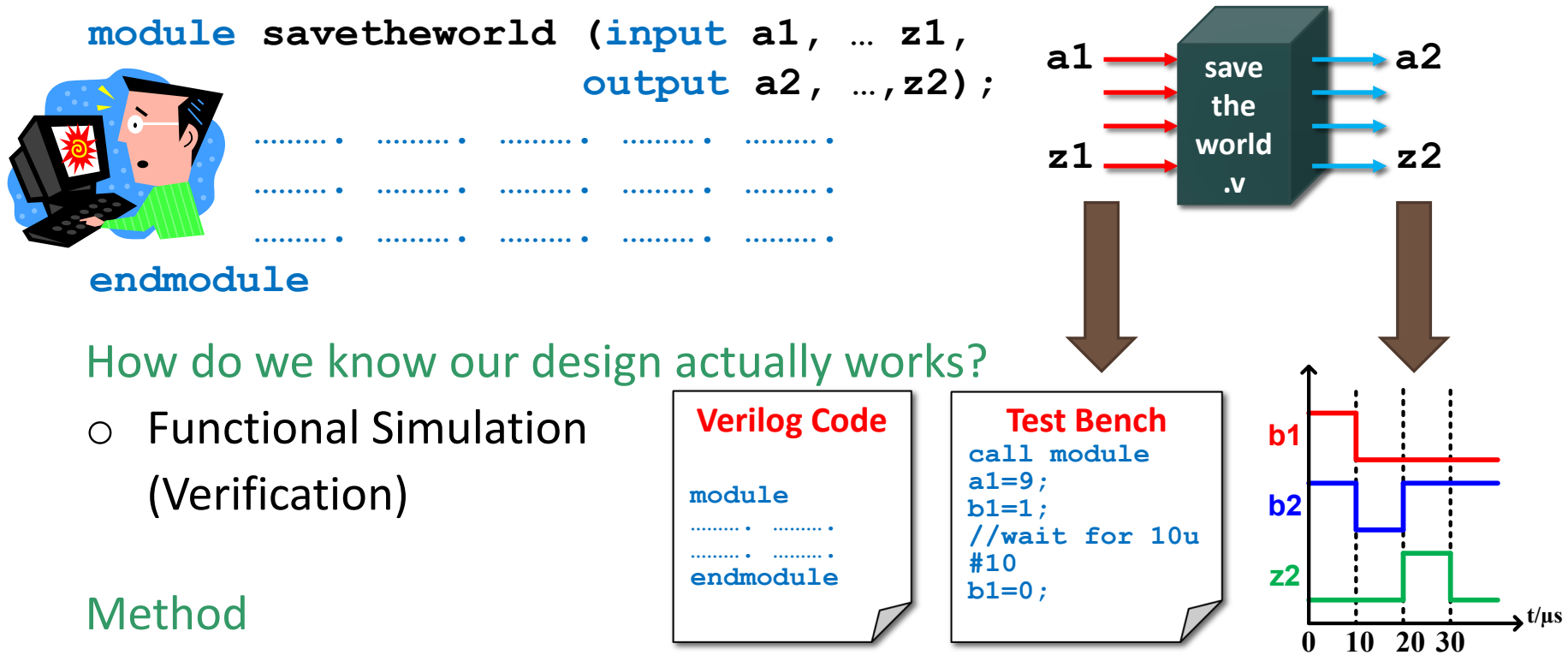

Testbench Example

```
module mux21( input s,  
              input [1:0] d,  
              output y);  
    assign y = s ? d[1] : d[0];  
endmodule
```

```
module mux_test();  
  
    reg [1:0] ip = 0;  
    reg sel = 0;  
    wire op;  
  
    mux21 dut (sel, ip, op);  
  
    initial begin  
        ip = 2'b10;  
        sel = 1'b0;  
        #10; //wait 10 time units  
    end  
  
endmodule
```

