

EE2026

Digital Design

BOOLEAN FUNCTION MINIMIZATION

Massimo ALIOTO

Dept of Electrical and Computer Engineering

Email: massimo.alioto@nus.edu.sg

Get to know the latest silicon system breakthroughs from our labs in 1-minute video demos




Outline

- Gate-level design and Boolean function minimization
- Karnaugh maps (K-maps)
- Boolean function simplification using K-maps
- Considerations on gate-level implementation

Gate-Level Design with Minimum Complexity

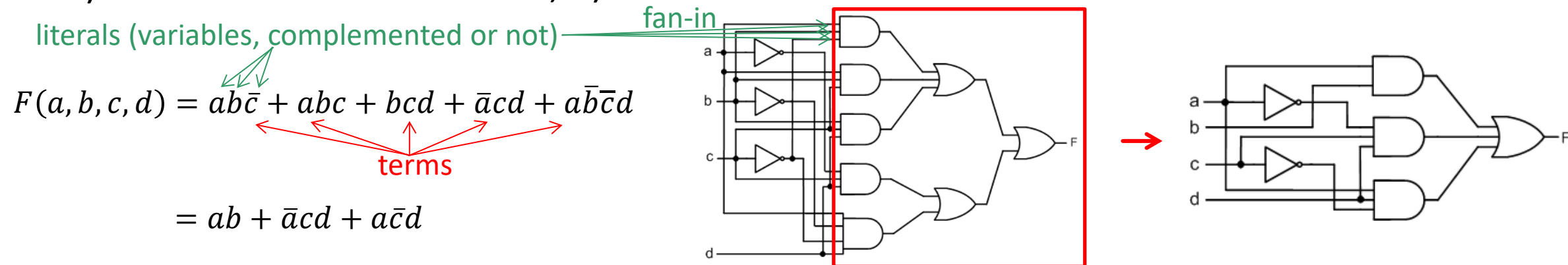- Minimize Boolean function before gate-level design is crucial
 - Lower cost (fit smaller FPGA), faster (fewer gate delays), lower power (fewer gates)
 - Reduce Boolean function to its minimal form
- Definition of simplified Boolean Function (recap)
 - 1) Minimal number of **terms**, 2) minimal number of **literals** in each term



- Impact on gate-level implementation
 - 1) Minimal gate count, 2) minimal fan-in in each logic gate (gate complexity)

Karnaugh Maps (K-Maps)

- K-map is a diagram that consists of a number of squares, each representing one SOP minterm (or POS maxterm) of a Boolean function
 - The SOP form (POS) can be expressed as a sum of minterms (maxterms) in the map
 - n-variable Boolean function has maximum 2^n minterms (maxterms)

Two-variable K-map:
(maximum 4 minterms)

		B	
		\bar{B}	B
A	\bar{A}	$\bar{A}\bar{B}$	$\bar{A}B$
	A	$A\bar{B}$	AB

Red arrows point to the four squares with the label "squares".



		B	
		0	1
A	0	00	01
	1	10	11



		B	
		0	1
A	0	m_0	m_1
	1	m_2	m_3


$m_0 \rightarrow 00 \rightarrow \bar{A}\bar{B}$
 $m_1 \rightarrow 01 \rightarrow \bar{A}B$
 $m_2 \rightarrow 10 \rightarrow A\bar{B}$
 $m_3 \rightarrow 11 \rightarrow AB$

A red arrow points from the m_3 entry in the table to its corresponding minterm expression.

"0" → Literal **with** overbar
"1" → Literal **without** overbar

Convert Truth table → K-map

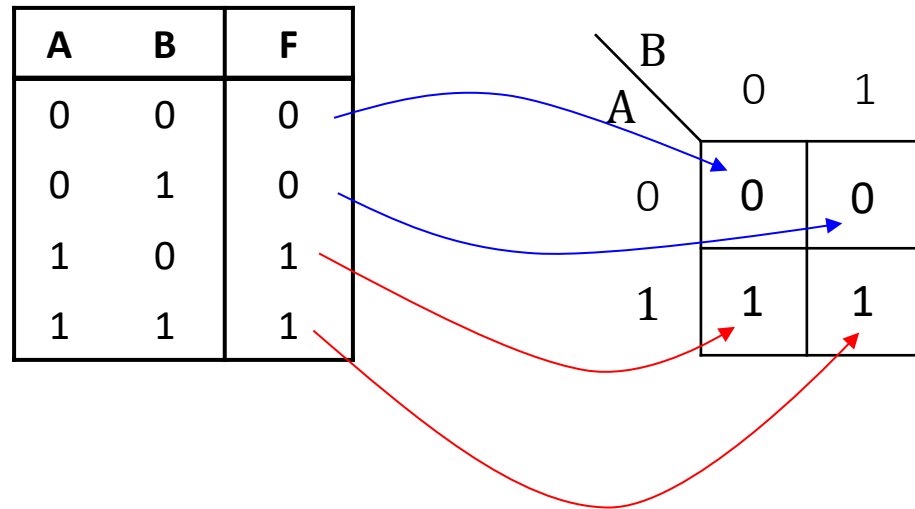- K-map is a two-dimensional representation of the truth table
 - Each row of in truth table corresponds to one square in the k-map
 - If the term in a row is a minterm of the function ($F=1$), place a “1” in the corresponding square of the K-map, otherwise (maxterm), place a “0”
 - Equivalent to truth table (just rearranged)



Three- and Four-Variable K-Maps

- In K-maps, any two adjacent squares differ by only one literal (“logically adjacent”), same in first-last row and column

Three-variable K-map

BC					
		$\bar{B}\bar{C}$	$\bar{B}C$	BC	$B\bar{C}$
A	\bar{A}	$\bar{A}\bar{B}\bar{C}$	$\bar{A}\bar{B}C$	$\bar{A}BC$	$\bar{A}B\bar{C}$
	A	$A\bar{B}\bar{C}$	$A\bar{B}C$	ABC	$AB\bar{C}$

↓

BC					
		00	01	11	10
A	0	000	001	011	010
	1	100	101	111	110

↓

BC					
		00	01	11	10
A	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6

Four-variable K-map


CD					
		00	01	11	10
AB	00	0000	0001	0011	0010
	01	0100	0101	0111	0110
	11	1100	1101	1111	1110
	10	1000	1001	1011	1010

↓

CD					
		00	01	11	10
AB	00	m_0	m_1	m_3	m_2
	01	m_4	m_5	m_7	m_6
	11	m_{12}	m_{13}	m_{15}	m_{14}
	10	m_8	m_9	m_{11}	m_{10}

Boolean Functions (Canonical) \leftrightarrow K-map

- Practice: represent function in canonical form through K-map
 - SOP: just place a “1” in squares representing its minterms

$$F = \overline{A}B + AB + A\overline{B}$$


		B	
		0	1
A	0	0	1
	1	1	1

Write the Boolean expression from the K-map

		B	
		0	1
A	0	0	1
	1	1	0

$$F = ?$$

in SOP: write F as sum of the minterms (squares with “1”)

$$F = \overline{A}B + A\overline{B}$$

Boolean Functions (Canonical) \leftrightarrow K-map

Represent the following function on K-map:

$$F = \bar{A}BC + AB\bar{C} + \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C}$$

BC A					
		00	01	11	10
0	1	1	1	0	
1	0	0	0	1	

$$F = \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}CD + A\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + A\bar{B}C\bar{D} + A\bar{B}\bar{C}D + \bar{A}\bar{B}\bar{C}\bar{D}$$

CD AB					
		00	01	11	10
00	1	0	1	1	
01	0	1	0	0	
11	1	0	0	0	
10	0	1	1	1	

Write the Boolean expression for the function in K-map:

BC A					
		00	01	11	10
0	1	0	0	0	
1	0	1	0	0	

$$F = ? \quad F = \bar{A} \cdot \bar{B} \cdot \bar{C} + A \cdot \bar{B} \cdot C$$

CD AB					
		00	01	11	10
00	0	1	0	0	
01	0	0	0	1	
11	0	1	0	0	
10	0	0	0	0	

$$F = ? \quad F = \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + A\bar{B}\bar{C}D$$

Boolean Functions \leftrightarrow K-map

- Practice: represent function in non-canonical form through K-map
 - No need to expand products to minterms (sums to maxterms)
 - Just identify (groups of) squares corresponding to each term

$$F = \bar{A}B + \overset{\text{red arrow}}{A}B\bar{C} + \bar{A}\overset{\text{red arrow}}{B}C$$

$$\overset{\text{red arrow}}{\bar{A}B} = \bar{A}B(C + \bar{C}) = \bar{A}BC + \bar{A}B\bar{C}$$

BC A	00	01	11	10
0	0	1	1	1
1	0	0	0	1

Or $\bar{A}B \rightarrow 01, C = 0 \text{ or } 1$

or just fill the truth table and derive the K-map


$$F = \overset{\text{red arrow}}{A} + \bar{A}\bar{B}\overset{\text{red arrow}}{C}D + B\bar{C}\bar{D}$$

CD AB	00	01	11	10
00	0	0	1	0
01	1	0	0	0
11	1	1	1	1
10	1	1	1	1

Boolean Function Simplification Using K-Maps

- Observation: 2 adjacent squares differ by one literal → simplified into 1

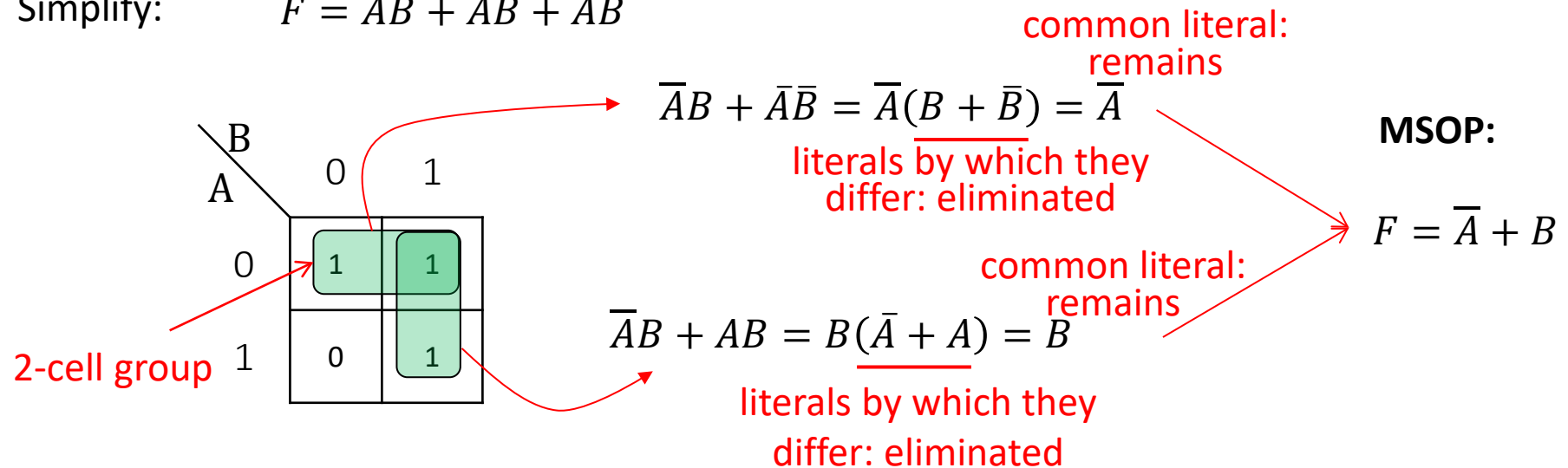Simplify: $F = \bar{A}B + AB + \bar{A}\bar{B}$



- Variable that is common remains
- Variable that changes is eliminated
- Check using Boolean manipulations

$$\begin{aligned} F &= \bar{A}B + AB + \bar{A}\bar{B} \\ &= \bar{A} + AB \\ &= \bar{A} + B \end{aligned}$$

Boolean Function Simplification Using K-Maps

Three-variables:

$$F = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + \underline{\bar{A}B\bar{C} + \bar{A}BC}$$

$$\downarrow$$

$$F = \bar{A} + B\bar{C}$$

$$\begin{aligned} \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC &\rightarrow \bar{A}\bar{B}(\bar{C} + C) + \bar{A}B(\bar{C} + C) \\ &\rightarrow \bar{A}\bar{B} + \bar{A}B \rightarrow \bar{A}(\bar{B} + B) \rightarrow \bar{A} \end{aligned}$$

$$\bar{A}B\bar{C} + \bar{A}BC \rightarrow (\bar{A} + \bar{A})B\bar{C} \rightarrow B\bar{C}$$

$$F = \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}B\bar{C} + \bar{A}BC + \underline{\bar{A}B\bar{C} + \bar{A}BC}$$

$$\downarrow$$

$$F = \bar{B} + \bar{A}\bar{C}$$

$$\begin{aligned} \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}B\bar{C} + \bar{A}BC &\rightarrow \bar{A}\bar{B}(C + \bar{C}) + \bar{A}B(\bar{C} + C) \\ &\quad (\bar{A} + \bar{A})\bar{B} \rightarrow \bar{B} \end{aligned}$$

$$\bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} \rightarrow \bar{A}(\bar{B} + B)\bar{C} \rightarrow \bar{A}\bar{C}$$

\bar{A} (B and C eliminated)

BC A	00	01	11	10
0	1	1	1	1
1	0	0	0	1

$B\bar{C}$ (A eliminated)

\bar{B} (A and C eliminated)

BC A	00	01	11	10
0	1	1	0	1
1	1	1	0	0

$\bar{A}\bar{C}$ (B is eliminated)

- Group adjacent cells where only one variable changes, so that it can be eliminated

Boolean Function Simplification Using K-Maps

Four-variables:

$$F = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}CD + \bar{A}B\bar{C}D + \bar{A}BCD \\ + A\bar{B}\bar{C}D + ABCD + A\bar{B}\bar{C}\bar{D} + A\bar{B}CD$$





$$F = \bar{B}\bar{C}\bar{D} + BD + CD$$

$$F = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}D + \bar{A}BCD \\ + A\bar{B}\bar{C}D + ABCD + A\bar{B}\bar{C}\bar{D} + A\bar{B}C\bar{D}$$



$$F = \bar{B}\bar{D} + BD$$

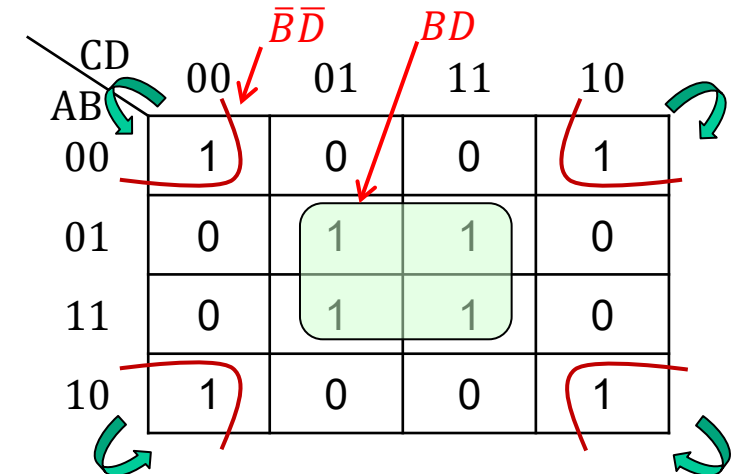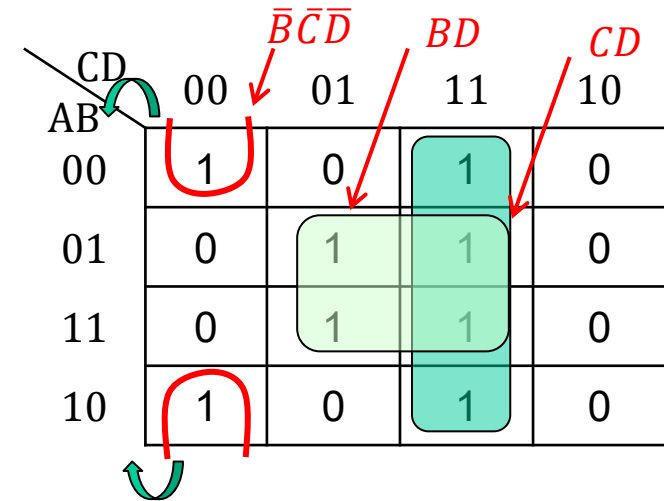

Boolean Function Simplification Using K-Maps

Four-variables:

$$F = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D \\ + \bar{A}BCD + \bar{A}BC\bar{D} + A\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}D \\ + ABCD + ABC\bar{D} + A\bar{B}C\bar{D} + A\bar{B}C\bar{D}$$

↓

$$F = B + \bar{D}$$


CD \ AB	00	01	11	10
00	1	0	0	1
01	1	1	1	1
11	1	1	1	1
10	1	0	0	1

Grouping rules:

- Group the squares that only contains “1”
- Groups must be either horizontal or vertical (diagonal is invalid)
- Group size is always 2^n , that is, 2, 4, 8, ...
- Group should be as large as possible (contains as many as squares with “1” as possible)
- Each square with “1” must be part of a group if possible
- Simplified term retains those variables that don’t change value
- Variables that change value in the group are eliminated

Invalid Groupings


CD \ AB	00	01	11	10
00	1	0	1	0
01	0	1	1	0
11	0	1	1	0
10	1	0	1	0

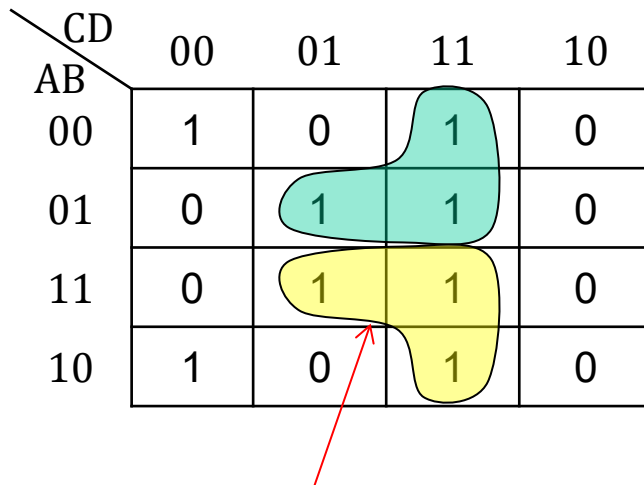

Squares in the group are not in power of two

two variable change value

CD \ AB	00	01	11	10
00	0	1	0	1
01	1	0	0	1
11	0	1	1	1
10	0	1	1	1

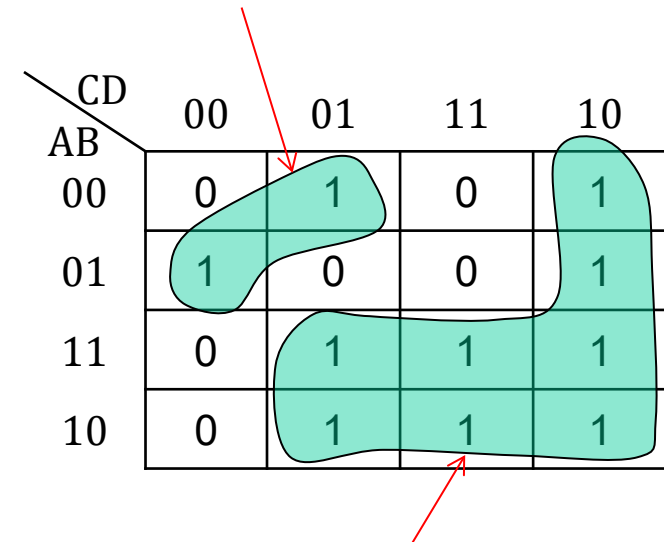

not horizontal or vertical

Don't-Care Conditions

- So far, all combination of input variables assumed to be valid
 - n-variable Boolean function $\rightarrow 2^n$ input combinations to be considered
- In practical cases, some variable combinations never appear
 - Example: BCD code (0...9 valid, 10...15 invalid)
 - Example: not all processor words point at existing instructions
- Invalid input values are called *don't-care conditions*
 - Marked with "X" or "-" in K-map
 - For minimization, X can take either "1" or "0"
 - Can choose freely, based on pure convenience for simplification purposes
 - Each d.c.c. is set independently from all others

Binary-Coded Decimal (BCD)

Decimal Symbol	BCD Digit
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001

Minimization with Don't-Care Conditions: SOP

- Choose value that allows to expand groups of squares as much as possible
 - Do not do it otherwise (it adds further terms, more complex)

$$F = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}BC\bar{D} \\ + A\bar{B}\bar{C}\bar{D} + ABC\bar{D} + A\bar{B}C\bar{D} + A\bar{B}C\bar{D}$$



$$F = B + \bar{D}$$

*Treat X = 1 and group the squares as usual

CD \ AB	00	01	11	10
00	1	0	0	1
01	X	1	X	1
11	X	1	X	1
10	1	0	0	1

Assume X = 1

Minimization with K-Maps: POS

- Dual procedure compared to SOP (swap 0-1, swap products with sums)
 - Group the squares that only contains "0"
 - Form an OR term (sum) for each group, instead of a product
 - Value "1", instead of "0", represent complement of the variable
 - Follow similar grouping rules that we discovered in SOP

$$\begin{aligned}
 F &= (A + B + C + \bar{D})(A + B + \bar{C} + D) \\
 &\quad (A + \bar{B} + C + D)(A + \bar{B} + \bar{C} + D) \\
 &\quad (\bar{A} + \bar{B} + C + D)(\bar{A} + \bar{B} + \bar{C} + D) \\
 &\quad (\bar{A} + B + C + \bar{D})(\bar{A} + B + \bar{C} + D)
 \end{aligned}$$



$$F = (B + C + \bar{D}) \cdot (\bar{C} + D) \cdot (\bar{B} + D)$$

$$(A + B + C + \bar{D}) \cdot (\bar{A} + B + C + \bar{D})$$

$$= A\bar{A} + A \cdot (B + C + \bar{D}) + (B + C + \bar{D}) \cdot \bar{A} + (B + C + \bar{D}) \cdot (B + C + \bar{D}) = (B + C + \bar{D})$$

maxterm-input correspondence: complement literals if 1

CD \ AB	00	01	11	10
00	1	0	1	0
01	0	1	1	0
11	0	1	1	0
10	1	0	1	0

- No way to know if SOP is simpler than POS upfront (or vice versa)


→ Need to implement both and compare terms and literals

A Systematic Procedure to Minimize with K-Maps


- Some terminology
 - Implicant, prime implicant and essential implicant
- Implicant of a Boolean function
 - Each product term in SOP is called an implicant of the function

Example 1

Implicants


$$F(a, b, c) = ab + \bar{a}\bar{b}c + \bar{a}b\bar{c} + \bar{c} + abc$$

Literals



Example 2

		BC			
		00	01	11	10
A	0	1	1	0	0
	1	1	1	1	0

How many implicants?

A Systematic Procedure to Minimize with K-Maps


- Prime implicant
 - Implicant that cannot be combined with another term to eliminate a variable
 - Graphically: it cannot be enclosed within a larger square/rectangle in K-map

Example 1

$$F = AB + \overbrace{ABC}^{\text{non-prime implicant (already contained in } AB \text{ or } BC)} + BC$$

↔
prime implicants

Example 2

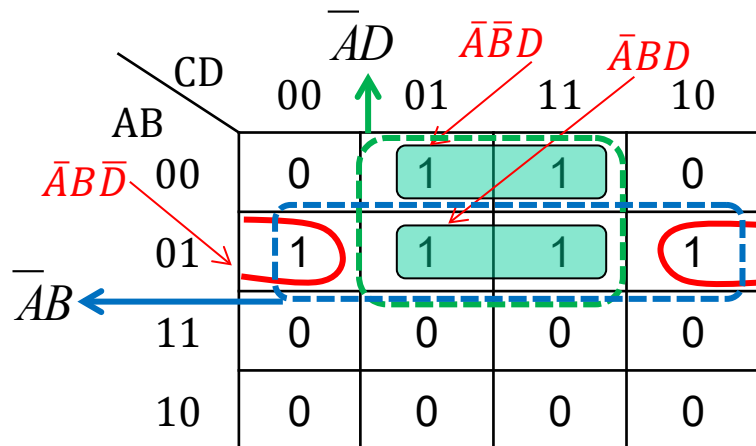

$\overline{A}\overline{B}D$, $\overline{A}BD$ and $\overline{A}B\overline{D}$


are implicants, but not prime implicants
(can be grouped into larger groups of 4)

$\overline{A}D$ and $\overline{A}B$ are essential prime implicants


graphically: prime implicant grouping
cannot be expanded further (but could
overlap with other prime implicants)

A Systematic Procedure to Minimize with K-Maps

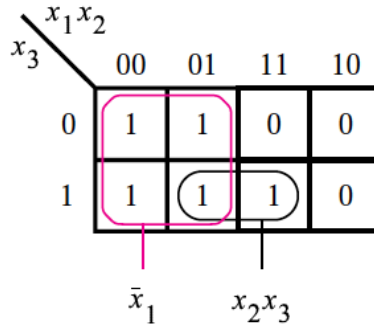- Essential prime implicant
 - Prime implicant that is not included in any other prime implicant



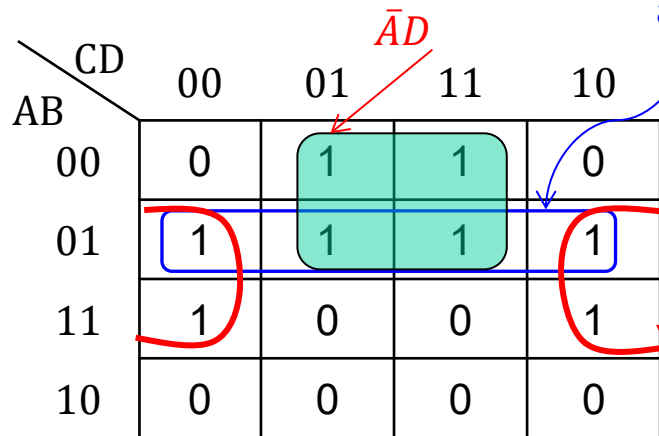Both \bar{x}_1 and $x_2 x_3$ are essential prime implicants



Prime implicant (not an essential prime implicant, already covered by the other two implicants)

Essential prime implicants: $\bar{A}D$ and $B\bar{D}$

graphically: essential prime implicant is needed to cover some 1 (i.e., it does not completely overlap with other implicants)

A Systematic Procedure to Minimize with K-Maps

- Resulting systematic procedure for K-map minimization in SOP form
 - Finding all prime implicants of the function
 - Select essential prime implicants (expand groups as much as possible)
 - Find a minimal subset of these prime implicants that covers all of the minterms of the function

select the essential prime implicant
with minimum set of prime implicants

CD \ AB	00	01	11	10
00	1	0	1	1
01	1	0	1	0
11	1	1	1	1
10	0	0	0	0


essential
prime implicant



CD \ AB	00	01	11	10
00	1	0	1	1
01	1	0	1	0
11	1	1	1	1
10	0	0	0	0

all implicants including
one essential prime implicant

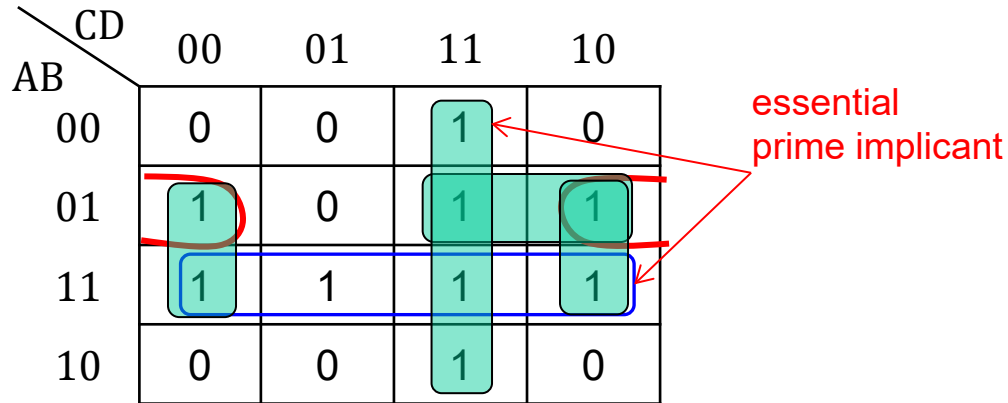
A Systematic Procedure to Minimize with K-Maps




All implicants including
two essential prime implicant



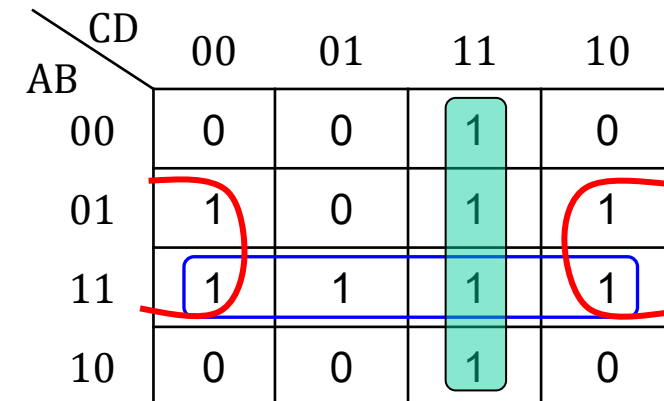select the essential prime implicant
with minimum set of prime implicants



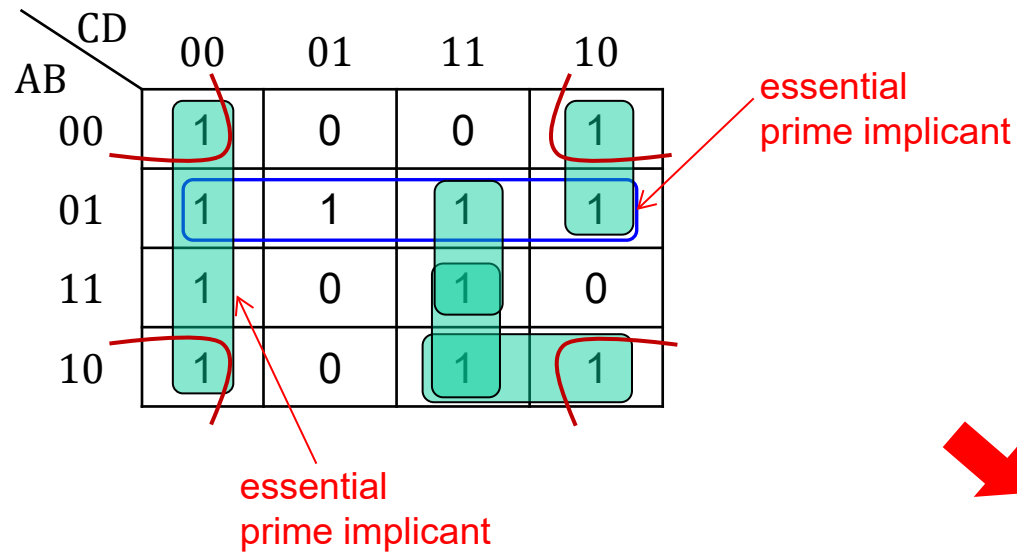
A Systematic Procedure to Minimize with K-Maps




all implicants including
two essential prime implicant



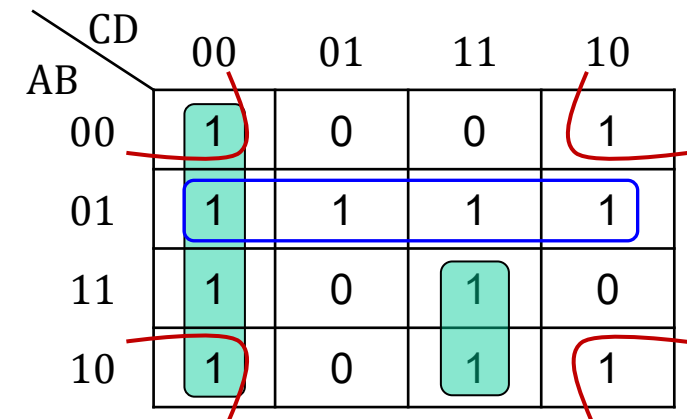select the essential prime implicant
with minimum set of prime implicants



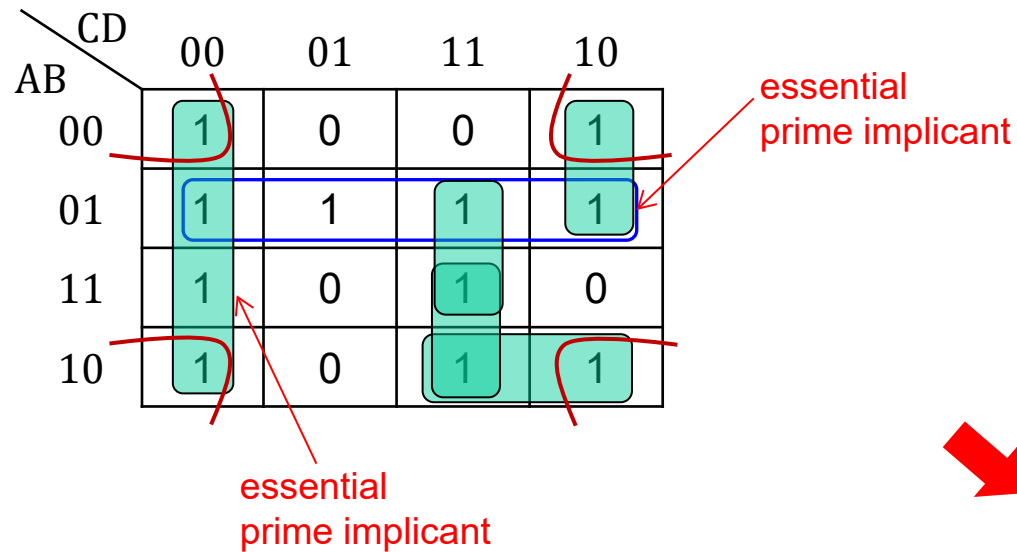A Systematic Procedure to Minimize with K-Maps



all implicants including
two essential prime implicant



select the essential prime implicant
with minimum set of prime implicants

